



University of California, Irvine

EECS 270A – Advanced Analog IC Design - 1

Fall 2021

Final Project

University of California, Irvine

Prof. Hamidreza Aghasi

Submitted by:

Ranjith Dhananjaya – 38807776

rdhananj@uci.edu

December 10, 2021

Contents:

- Design problem
- Design approach and calculations
- Simulation results
- Summary

Design problem:

Design an amplifier (with more than one stage) that satisfies the listed requirements:

- (Gain-bandwidth product) $GBW > 210\text{e}9$
- $R_{in} > 500\text{ k}\Omega$
- $R_{out} < 150\text{ }\Omega$
- DC Power Consumption $< 18\text{ mW}$
- Output Voltage Swing $> 2.4\text{ V}_{pp}$
- $V_{dd} < 3.6$

Design approach:


The amplifier was designed on paper and then simulated on Cadence. The details of the design are as shown below:

Design Steps

(Page 1)

For $PM \geq 60^\circ$, $C_c \geq 0.22 C_L$

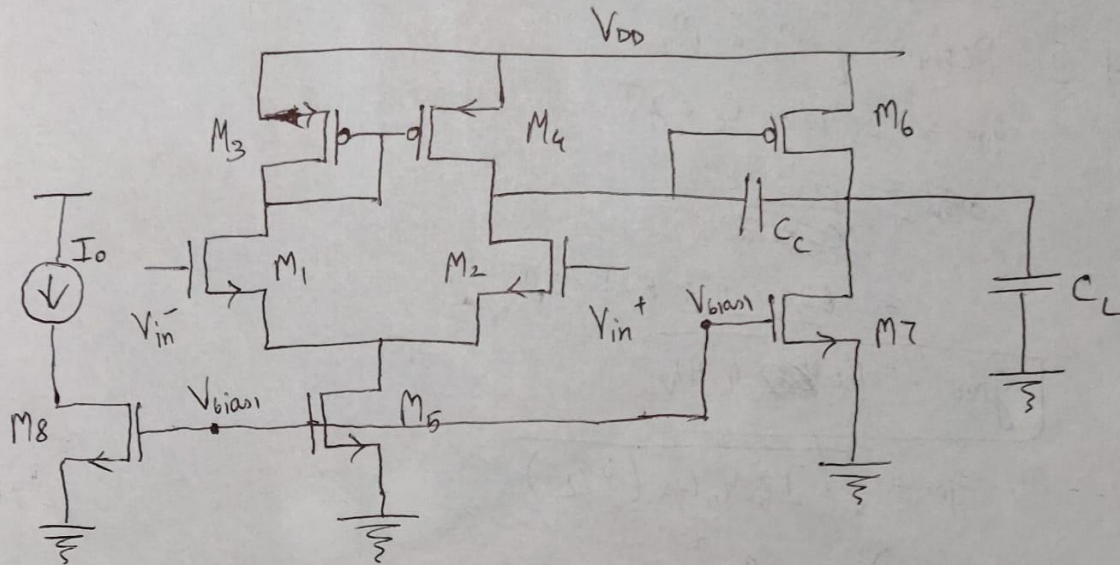Topology: Differential Pair with Active Load followed by common source stage



Let $GBW = 30 \text{ MHz}$

$PM \geq 60^\circ$

$SR = 10 \text{ V}/\mu\text{s}$

$ICMR(+) = 1.6 \text{ V}$

$ICMR(-) = 0.8 \text{ V}$

$C_L = 2 \text{ pF}$

Power dissipation $\leq 18 \text{ mW}$

Also, from simulation, I found the values of:

$\mu_p C_{ox} = 0.152 \text{ m}$

$\mu_n C_{ox} = 30.46 \text{ m}$

$B_{effp} = 3.812 \text{ m}$

$B_{effn} = 11.67 \text{ m}$

$L = 45 \text{ nm}$

$W = 1.125 \mu\text{m}$

Let $V_{DD} = 1.8 \text{ V}$

Process = 45nm

Step ① $C_L = 2 \text{ pF}$

$C_c \geq 0.22 \times 2 \text{ pF}$

$C_c \geq 0.44 \text{ pF}$

$C_c = 800 \text{ fF}$

Step ②

$$SR = \frac{I_5}{C_c}$$

$$I_5 = SR \times C_c$$

$$= \frac{20V}{\mu s} \times 800fF$$

$$I_5 = 20 \mu A$$

Step ③ Design of M_1 & M_2

$$g_{m1} = GBW \times C_c \times 2\pi$$

~~$$GBW = \frac{g_{m1}}{C_c \times 2\pi}$$~~

$$= 30 \times 10^6 \times 800f \times 2\pi$$

$$g_{m1} = 160 \mu A/V$$


$$g_m = \sqrt{2 I_D \mu_n C_{ox} (W/L)}$$

$$\Rightarrow (W/L) = \frac{g_{m1}^2}{2 I_D \mu_n C_{ox}}$$

$$(W/L)_{1,2} = \frac{160^2 \times 10^{-12}}{20 \times 0.46 m \times 10^{-6}}$$

$$= 2.78 \approx \underline{\underline{3}}$$

Step ④

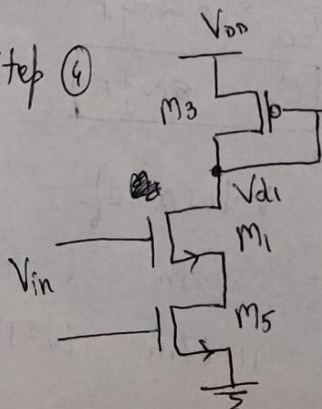

If we increase V_{in} , M_1 enters triode.
For M_1 to be in saturation,

$$V_{di} \geq V_{g1} - V_{t1}$$

$$V_{g1} \leq V_{di} + V_{t1}$$

$$\Rightarrow V_{in} \leq V_{di} + V_{t1}$$

$$V_{in(max)} = V_{d1} + V_{t1} \quad \text{--- (1)}$$

$$V_{d1} = V_{DD} - V_{sg3}$$

$$V_{d1} = V_{DD} - \left[\sqrt{\frac{2 I_{D3}}{\beta_P}} + |V_{t3}| \right]$$

$$I_3 = \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$I_3 = \frac{\beta_P}{2} (V_{GS} - V_t)^2$$

$$\Rightarrow V_{GS} = \sqrt{\frac{2 I_3}{\beta_P}} + |V_{t3}|$$

From (1),

$$ICMR(+) \leq V_{OL(min)} + V_{t1(min)}$$

From (1) & (2),

$$\Rightarrow ICMR(+) \leq \left[V_{DD} - \left(\sqrt{\frac{2 I_{D3}}{\beta_P}} + |V_{t3}| \right) \right]_{min} + V_{t1 min}$$

$$\Rightarrow ICMR(+) \leq V_{DD} - \sqrt{\frac{2 I_{D3}}{\beta_{P3}}} - |V_{t3}|_{max} + V_{t1 min}$$

$$\Rightarrow \frac{2 I_{D3}}{\beta_3} = \left(V_{DD} - ICMR_{max} - |V_{t3}|_{max} + V_{t1 min} \right)^2$$

$$\Rightarrow \frac{2 I_{D3}}{\mu_P C_{ox} (W/L)_3} = V_{DD} - ICMR - |V_{t3}|_{max} + V_{t1 min}$$

$$(W/L)_3 = \frac{2 I_{D3}}{\mu_P C_{ox} [V_{DD} - ICMR - V_{t3 max} + V_{t1 min}]^2}$$

From simulation, $V_{t3 max} = 0.51$


$V_{t1 min} = 0.47$

$$\therefore (W/L)_3 = \frac{20 \mu A}{0.152 m [1.8 - 1.6 - 0.51 + 0.47]^2}$$

$$\boxed{(W/L)_3 = 4.55 \approx 5}$$

Step ⑤ Design of M_5

Page 4

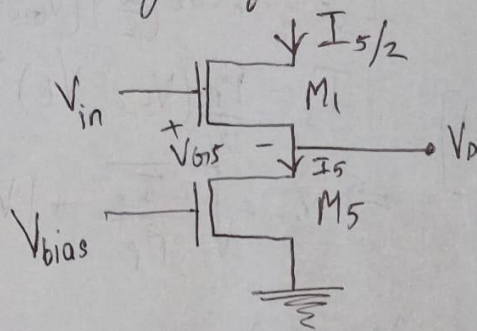

$$V_{D5} > V_g - V_t$$

M_5 enters triode

$V_{Dsat} \rightarrow M_5$ to be saturation

$$V_{in(min)} \geq V_{gs1} + V_{Dsat}$$

$$ICMR_{min(-)} \geq V_{gs1(max)} + V_{Dsat(fixed)}$$

$$\Rightarrow ICMR(-) \geq \left[\sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t1} \right]_{max} + V_{Dsat}$$

$$\Rightarrow ICMR(-) \geq \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t1(max)} + V_{Dsat}$$

$$V_{Dsat} \geq ICMR(-) - \sqrt{\frac{2I_{D1}}{\beta_1}} - V_{t1(max)}$$

$$V_{Dsat} \geq 0.8 - \sqrt{\frac{2 \times 104}{0.46m \times 31}} - V_{t1(max)}$$

$$\text{From simulation } V_{t1(max)} = 0.59$$

$$V_{Dsat} \geq 0.8 - 0.12 - 0.59$$

$$V_{Dsat} \geq 90 \text{ mV}$$

$$V_{Dsat} = \underline{\underline{150 \text{ mV}}}$$

$$I_{D5} = \frac{1}{2} \mu_n C_{ox} (W/L)_5 V_{Dsat}^2$$

$$(W/L)_5 = 3.86 \approx 4$$

Step ⑥ Design of M_6 for PM of 60° , $g_{m6} \geq 10g_{m1}$

$$g_{m6} \geq 10 \times 160 \mu$$

$$g_{m6} \geq 1600 \mu$$

$$V_{DS3} = V_{DS4} = V_{DS6}$$

$$V_{GS3} = V_{GS4} = V_{GS6}$$

$$\frac{(W/L)_6}{(W/L)_4} = \frac{I_6}{I_4} \Rightarrow \frac{(W/L)_6}{(W/L)_4} = \frac{g_{m6}}{g_{m4}}$$

$$g_{m4} = \sqrt{2 I_D \cdot \mu_p C_{ox} (W/L)_4}$$

$$g_{m4} = \sqrt{20 \mu \times 0.152 \text{ m} \times 4}$$

$$g_{m4} = \underline{\underline{110.27 \mu \text{ A/V}}}$$

$$(W/L)_6 = \frac{g_{m6}}{g_{m4}} (W/L)_4$$

$$= \frac{1600 \times 5}{110.27}$$

$$= 58.03$$

$$\boxed{(W/L)_6 \approx 59}$$

Step ⑦ Design of M_7

(Page 6)


$$\frac{I_6}{I_4} = \frac{(w/L)_6}{(w/L)_4}$$

$$= \frac{(w/L)_6}{(w/L)_4} \times I_4$$

$$= \frac{59}{4} \times 10 \mu$$

$$= 147.5 \mu$$

$$\boxed{I_6 = 150 \mu}$$

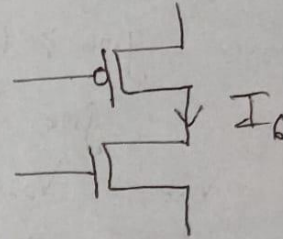

$$\frac{I_7}{I_5} = \frac{(w/L)_7}{(w/L)_5}$$

$$(w/L)_7 = \frac{I_7}{I_5} \cdot (w/L)_5$$

$$= \frac{150 \times 4}{20}$$

$$\boxed{(w/L)_7 = 30}$$

Summary:

① $(w/L)_{1,2} = 4 \rightarrow \frac{180}{45}$

② $(w/L)_{3,4} = 5 \rightarrow \frac{225}{45}$

③ $(w/L)_{5,8} = 4 \rightarrow \frac{180}{45}$

④ $(w/L)_6 = 59 \rightarrow \frac{2655}{45}$

⑤ $(w/L)_7 = 30 \rightarrow \frac{1350}{45}$

$I_6, I_7 = 150 \mu A$

DC Power consumption :

(Page 7)

$$P_{\text{DC}} = V \times I$$

$$= 1.8 \times [(150 \mu) + (20 \mu)]$$

$$= 1.8 \times [170 \mu]$$

$$= \underline{\underline{0.3 \text{ mW}}}$$

Output voltage Swing :

$$V_{\text{out(max)}} = V_{\text{DD}} - V_{\text{DSat(6)}}$$

$$= 1.8 - \sqrt{\frac{2 \cdot I_6}{K_6 \cdot (W/L)_6}}$$

$$= 1.8 - \sqrt{\frac{2 \times 150 \times 10^{-6}}{0.152 \text{ m} \times 59}}$$

$$= 1.8 - 0.1828$$

$$\therefore V_{\text{out(max)}} = \boxed{1.61 \text{ V}}$$

$$V_{\text{out(min)}} = \sqrt{\frac{2 \cdot I_7}{K_7 \cdot (W/L)_7}} = V_{\text{DSat(7)}}$$

$$= \sqrt{\frac{2 \times 150 \times 10^{-6}}{0.46 \text{ m} \times 30}}$$

$$V_{\text{out(min)}} = \underline{\underline{0.147 \text{ V}}}$$

$$\boxed{0.147 < V_{\text{out}} < 1.61}$$

Input Resistance

Page 8

$$R_{in} = r_{o1} \parallel r_{o3}$$
$$= \frac{1}{g_{ds1} + g_{ds3}}$$

⇒ From simulation: $g_{ds1} = 8.175 \mu$; $g_{ds3} = 7.835 \mu$

$$R_{in} = \frac{1}{(8.175 + 7.835) \mu}$$

$$\Rightarrow R_{in} = \underline{\underline{62.46 k\Omega}}$$

Output Resistance:

$$R_{out} = r_{o6} \parallel r_{o7}$$
$$= \frac{1}{g_{ds6} + g_{ds7}}$$


From simulation: $g_{ds6} = 115.8 \mu$; $g_{ds7} = 88.78 \mu$

$$\Rightarrow R_{out} = \frac{1}{(115.8 + 88.78) \mu}$$


$$\Rightarrow R_{out} = \underline{\underline{4.88 k\Omega}}$$

Simulation results:

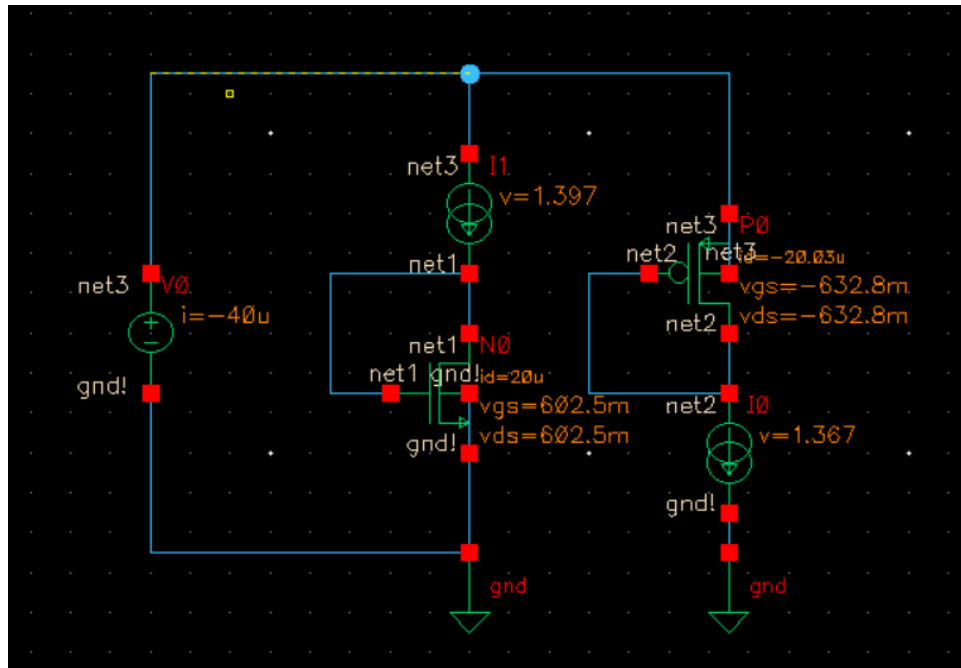
The circuit used to calculate the beta effective is as follows:



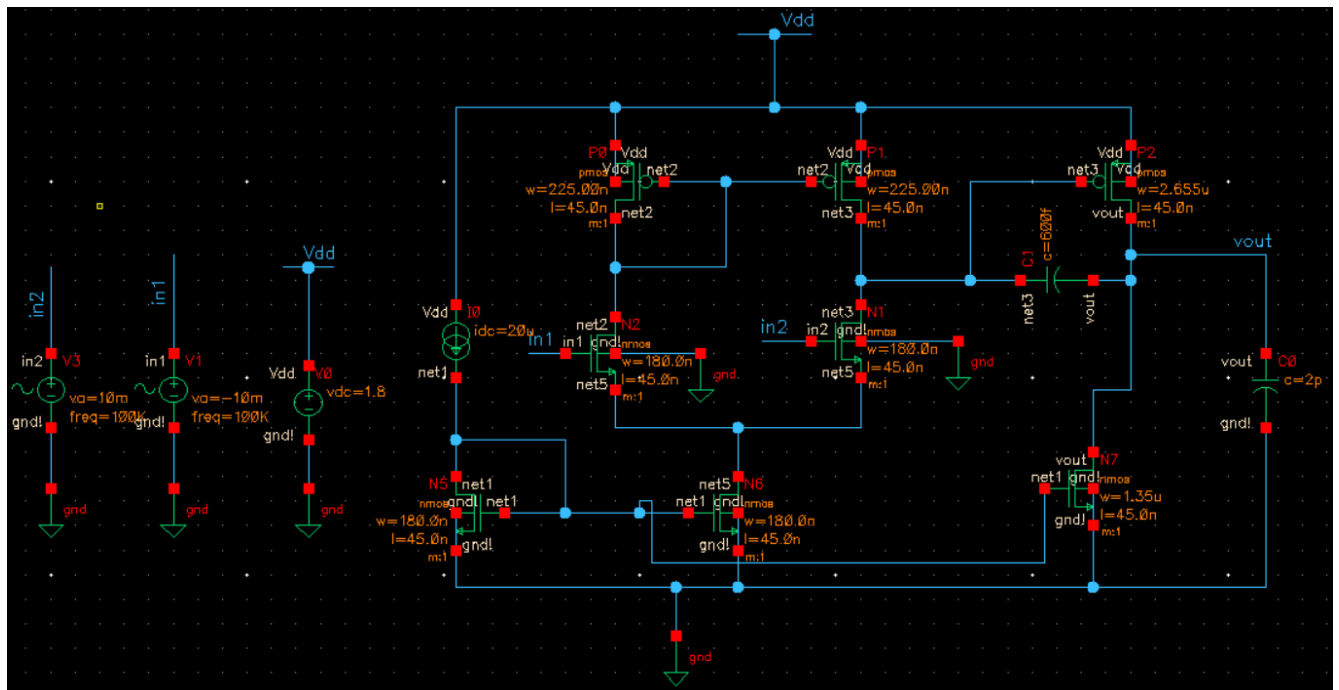
The amplifier circuit schematic is as shown: The dimensions of the transistors are depicted in the schematic.



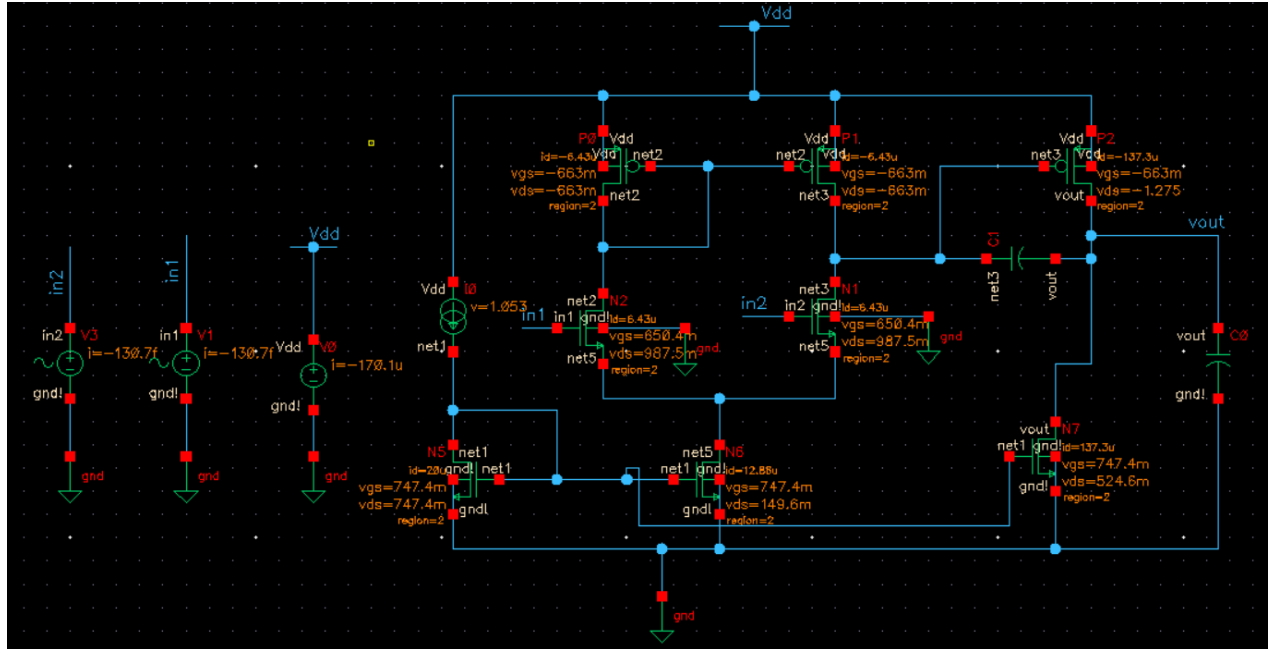
The DC analysis by setting ICMR = **0.8V** is as follows: All transistors are in region 2(saturation)



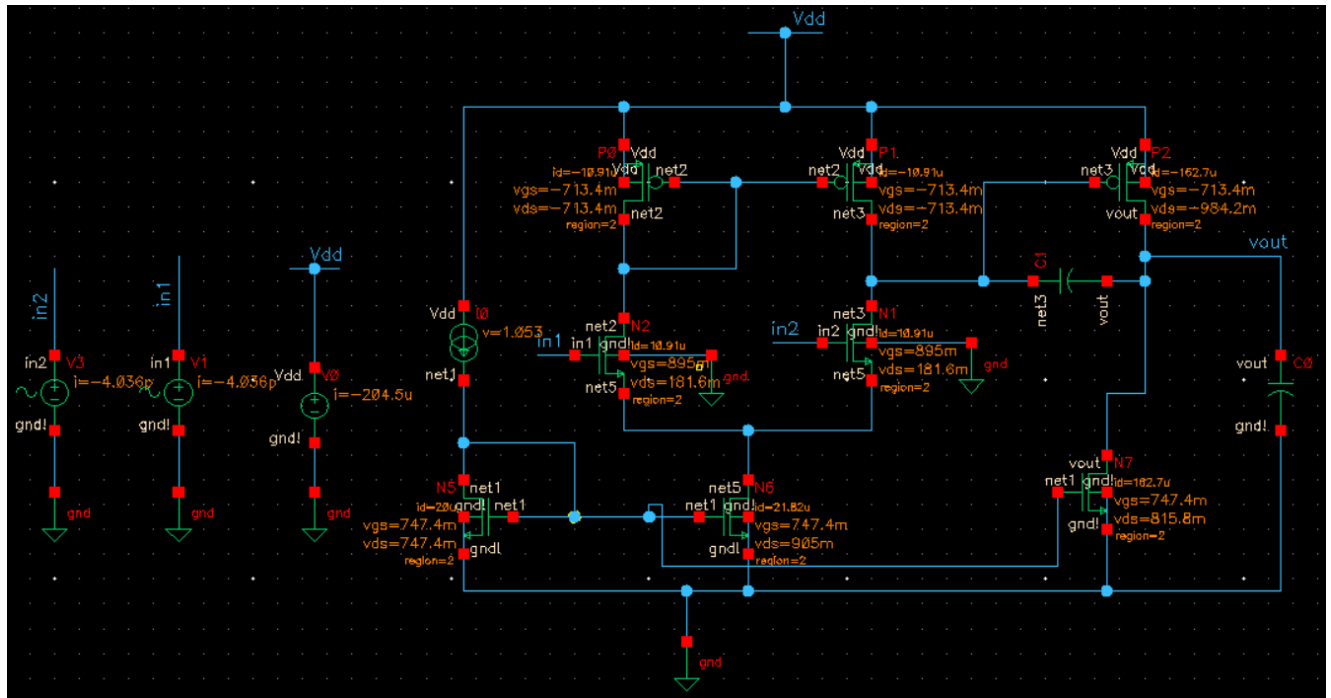The DC analysis by setting ICMR = **1.6V** is as follows: All transistors are in region 2(saturation)



Running transient analysis:

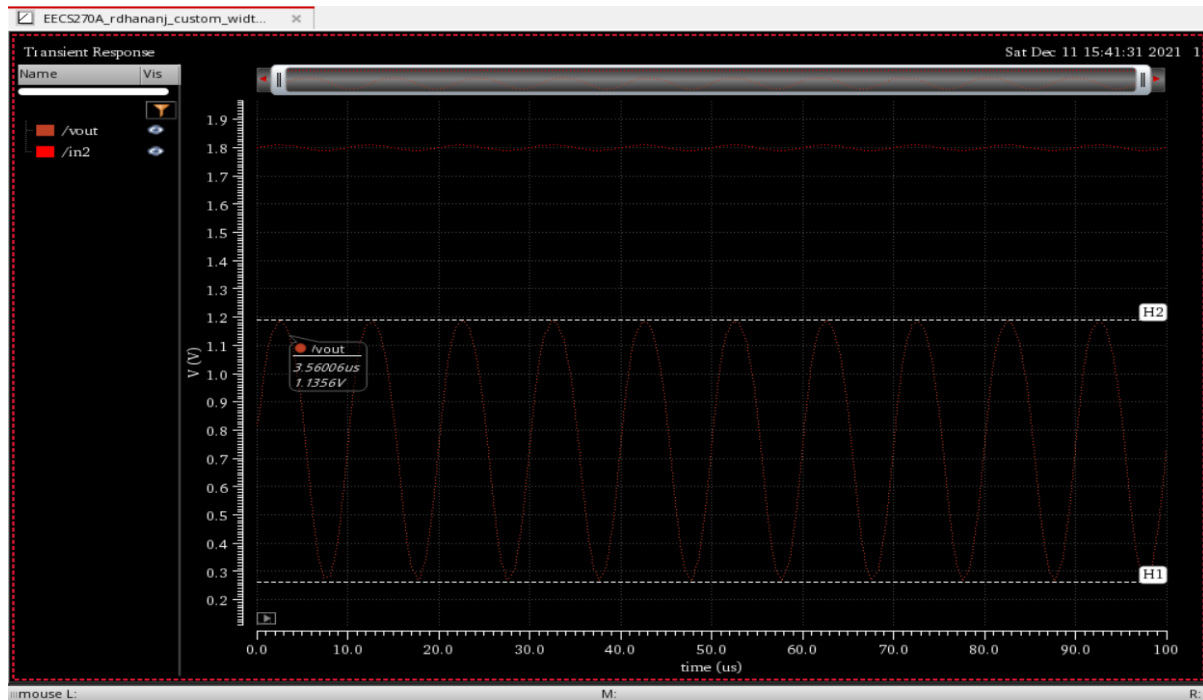

Input amplitude v_{in} (p to p) – 10mV

Input amplitude v_{ip} (p to p) – -10mV

Input frequency – 100kHz


Start time – 0

Stop time – 100us

Common mode voltage – 1.6V

Output amplitude (p to p) – 0.92V

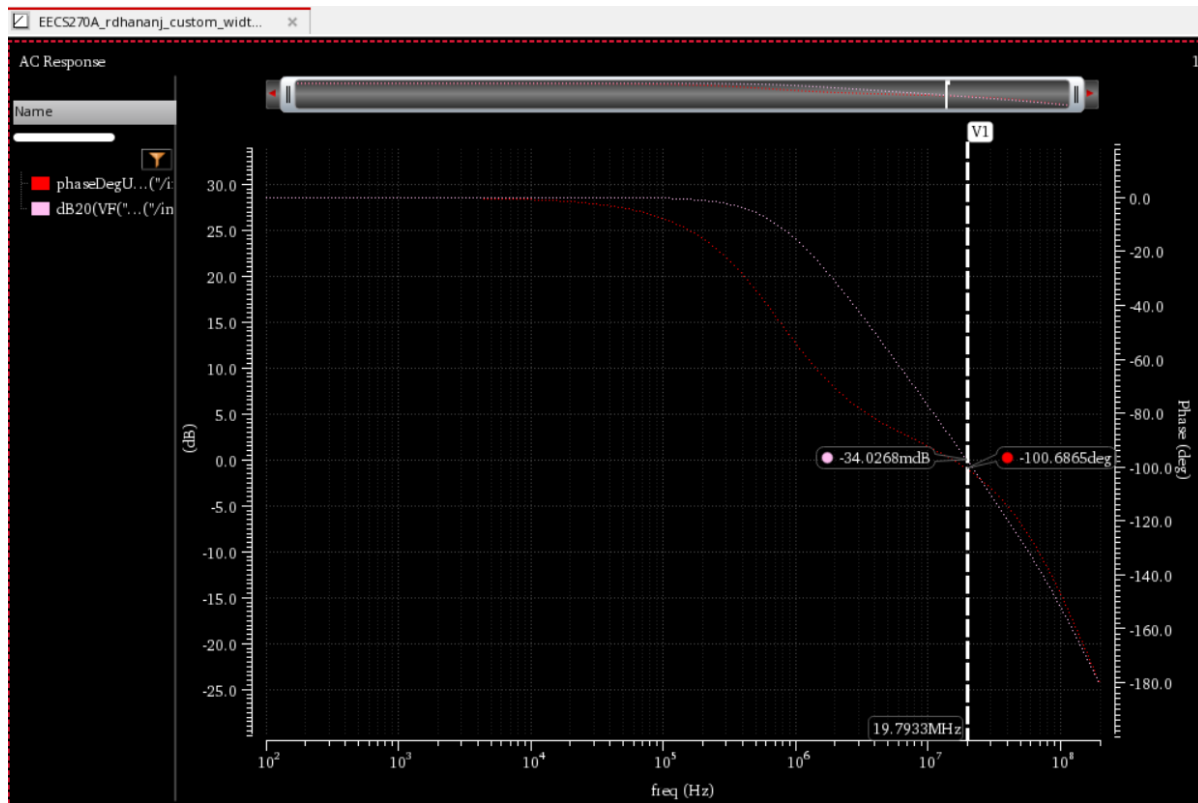
Running AC analysis and plotting the AC gain and phase:



It is observed that the GBW is 19.79MHz. Gain is about 27dB.

The phase margin is obtained as $180 - 100 = \underline{80 \text{ degrees}}$

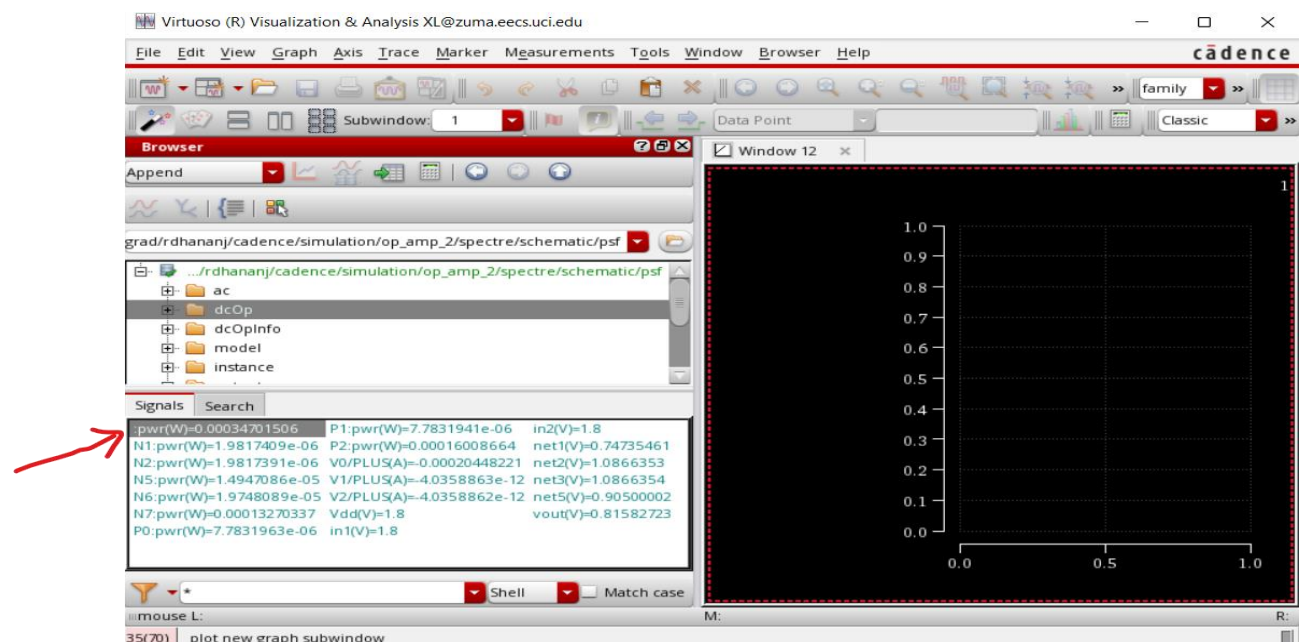Simulation to find the power dissipation:



From the simulation, we see that the power dissipation is 0.00034701506W which is approximately **0.35mW**

Summary:

Simulation results observed:

1. Gain Bandwidth Product - **19.79MHz**
2. Phase Margin – **80 degrees**
3. Gain – **27dB**
4. Power dissipation – **0.35mW**
5. Vdd used – **1.8V**
6. Rin – **62.46k ohm**
7. Rout – **4.88k ohm**